

## ***RF Components and Basic Concepts***

### ***1.18 - S-Parameters***

# Why we need S-parameters ?


- For high frequencies, it is convenient to describe a given network in terms of waves rather than voltages or currents. Microwave theory deals with **power quantities** rather than Voltage or current.

## ➤ Why ?

- Measurement of high-frequency voltages and currents in laboratory proves very difficult but measuring the average power is easier.
- Microwave theory models devices and circuits by parameters that can be obtained through the measurement of power quantities. These parameters are called scattering parameters or S-parameters.
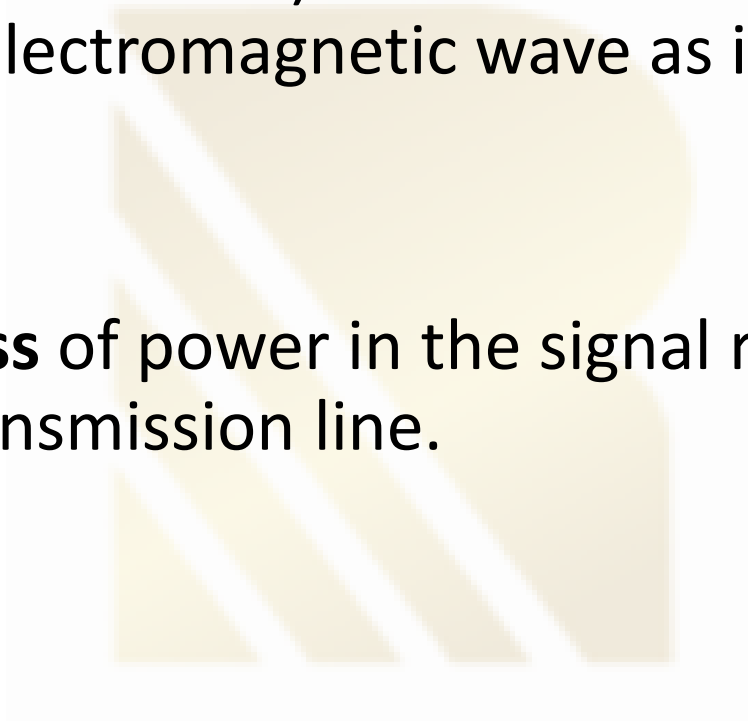
# Path Loss and Return Loss

- **Path loss** (or **path** attenuation) is the reduction in power density (attenuation) of an electromagnetic wave as it propagates through space.
- **Return loss** is the **loss** of power in the signal returned/reflected by a discontinuity in a transmission line.




# S-parameters

- We define S-Parameters for any two-port network.


- We have incident wave and reflected wave  
At the input ( $V_1^+$  and  $V_1^-$ )

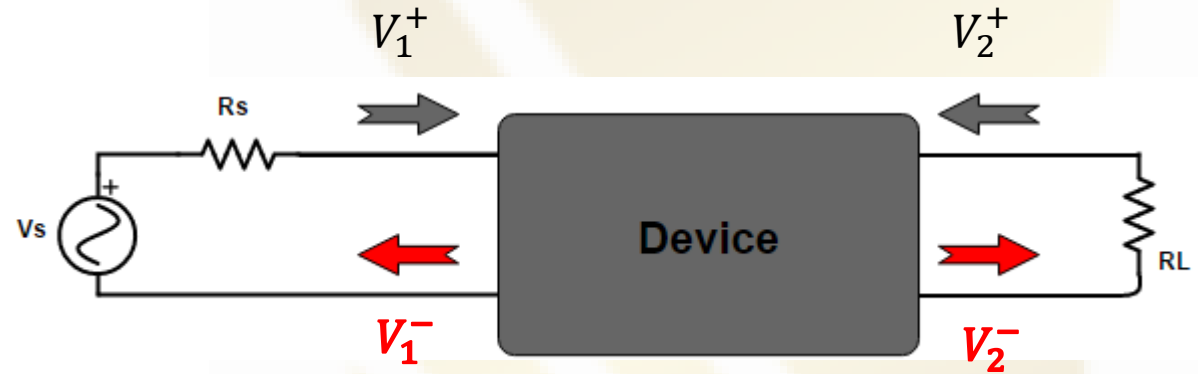- We have incident wave and reflected wave  
At the output ( $V_2^+$  and  $V_2^-$ )



# S-parameters

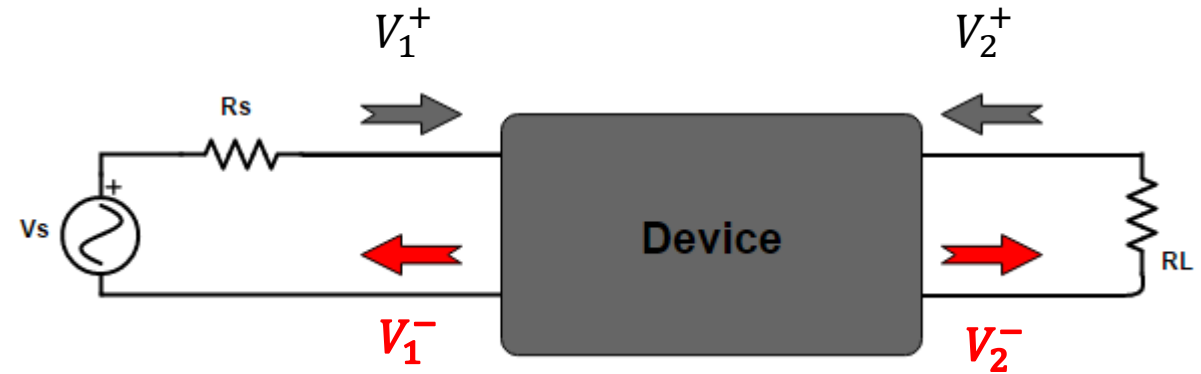- I.  $S_{11}$
- II.  $S_{12}$
- III.  $S_{21}$
- IV.  $S_{22}$




$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}. \quad b_1 = S_{11}a_1 + S_{12}a_2 \quad b_2 = S_{21}a_1 + S_{22}a_2.$$

S<sub>11</sub>

$$S_{11} = \frac{V_1^-}{V_1^+} \quad (V_2^+ = 0)$$

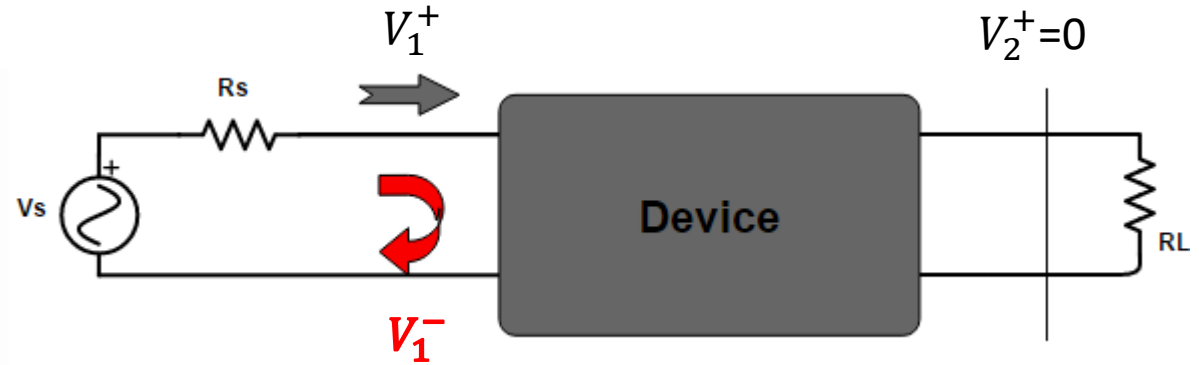S<sub>11</sub> shows the accuracy of  
Input matching.



$$S_{11} = 10 \log \left( \frac{V_1^-}{V_1^+} \right)$$


$$S_{11} \leq -15 \text{ dB}$$

# S12

$$S_{12} = \frac{V_1^-}{V_2^+} \quad (V_1^+ = 0)$$

- S12 shows the reverse isolation Of the circuit.
- Reverse isolation is a measure of how well a signal applied to the device output is "isolated" from its input.
- How much of the output signal couples to the input network.
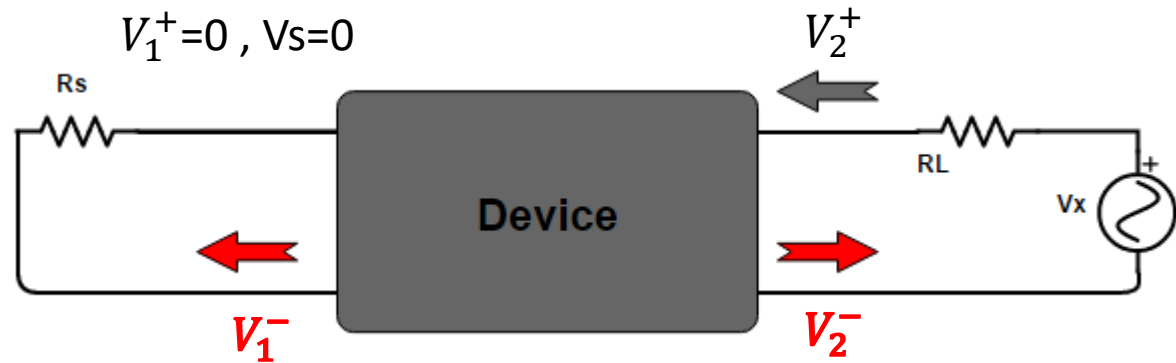
$$S_{12} = 10\log\left(\frac{V_1^-}{V_2^+}\right)$$




S22

$$S_{22} = \frac{V_2^-}{V_2^+} (V_1^+ = 0)$$

S22 shows the accuracy of  
output matching.
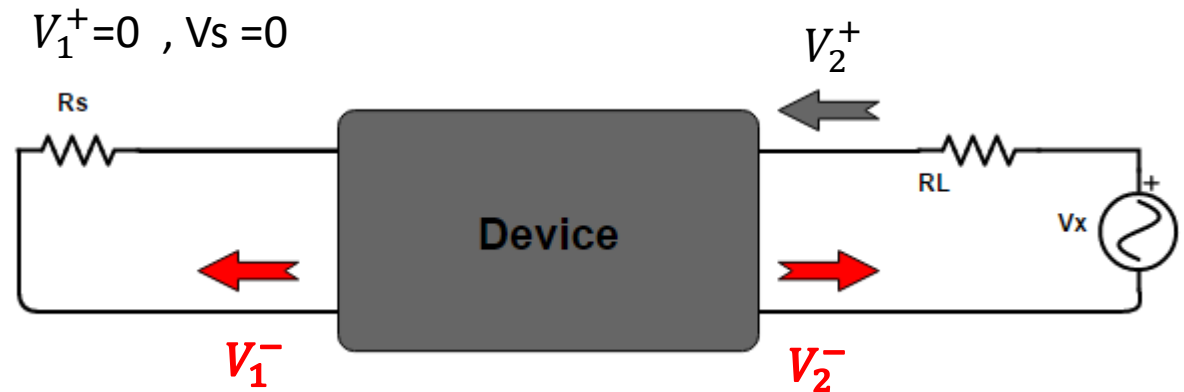
$$S_{22} = 10\log\left(\frac{V_2^-}{V_2^+}\right)$$



$$S_{22} \leq -15 \text{ dB}$$



S21

$$S_{21} = \frac{V_2^-}{V_1^+} (V_2^+ = 0)$$

S21 shows the **gain** of the Circuit.

$$S_{12} = 10\log\left(\frac{V_2^-}{V_1^+}\right)$$

