

RF Components and Basic Concepts


1.11 - Phase locked loop

PLL

- A phase-locked loop is a feedback system combining a voltage controlled oscillator (VCO) and a phase comparator so connected that the oscillator maintains a **constant phase angle** relative to a reference signal.
- Phase-locked loops can be used, for example, to generate stable output high frequency signals from a fixed low-frequency signal.

PLL

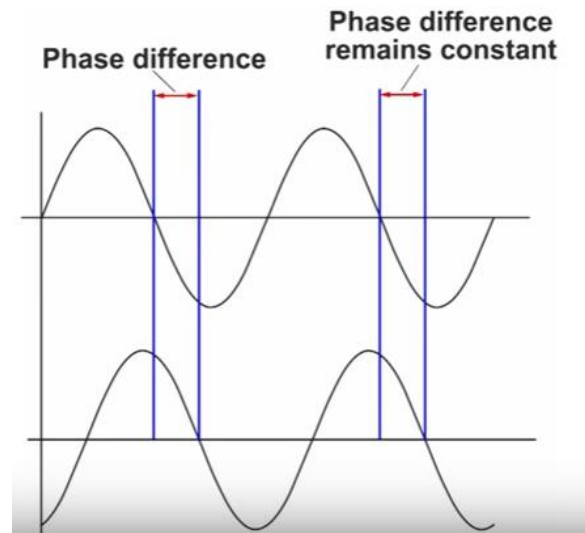- When phase between signals changes it means that they have different frequencies.
- When phase difference remains constant frequencies are equal.





Why we use PLL ?

VCO cannot produce stable high frequency carrier.

VCO is affected by temperature and noise.

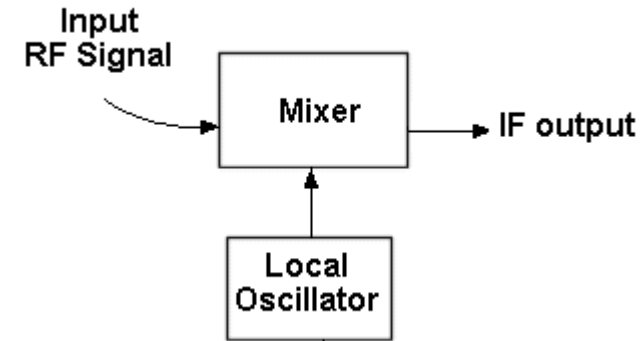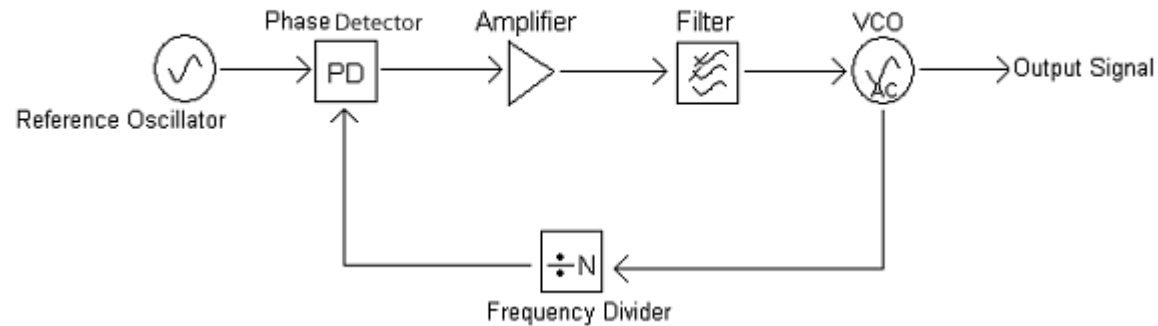
We need a reference with stable frequency and we force VCO to follow that reference.



Question ??

- Why we need PLL if we already have stable reference oscillator ?????
- Reference oscillator has low frequency such as crystal oscillator.




Reference Oscillator
Low Freq but stable
Crystall oscillator

How PLL works ?

